

Prelab Report

Group8: Muhan Li, Man Sun, Mingxiao An

I. PRELAB#1


$$C \frac{dv_{out}}{dt} = I = \frac{v_{in} - v_{out}}{R} \quad (1)$$

$$v_{out} + RC \frac{dv_{out}}{dt} = v_{in} \quad (2)$$

II. PRELAB#2

$$v_{out}(t) = -V_0 e^{-\frac{t}{RC}} + V_0 \quad (3)$$

III. PRELAB#3

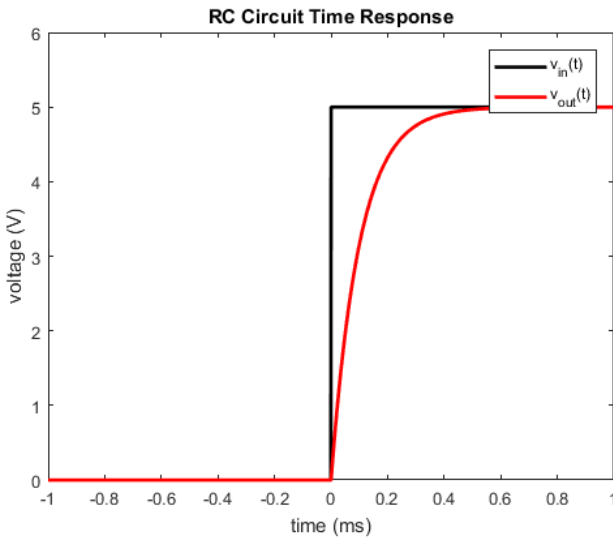


IV. PRELAB#4

$$v_{out}(0) = V_0 \quad (4)$$

$$v_{out}(t) = V_0 e^{-\frac{t}{RC}} \quad (5)$$

V. PRELAB#5

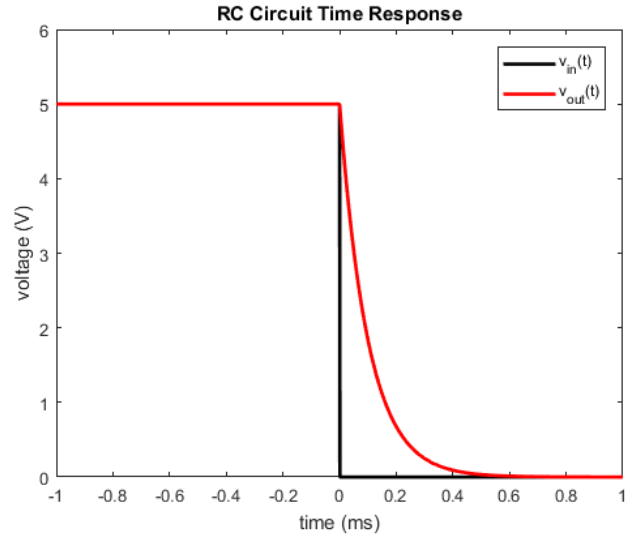

VI. PRELAB#6

a) Time Constant: $\tau = RC$

b) Rise Time:

10%-point: $e^{-\frac{t}{RC}} = 0.9, t = 0.1RC$;

90%-point: $e^{-\frac{t}{RC}} = 0.1, t = 2.3RC$;

rise time is $2.3RC - 0.1RC = 2.2RC$

c) Fall Time:

90%-point: $e^{-\frac{t}{RC}} = 0.9, t = 0.1RC$;

10%-point: $e^{-\frac{t}{RC}} = 0.1, t = 2.3RC$;


fall time is $2.3RC - 0.1RC = 2.2RC$

d) Delay Time:

90%-point: $e^{-\frac{t}{RC}} = 0.5, t = 0.69RC$;

delay time is $0.69RC$ for both R and C

VII. PRELAB#7

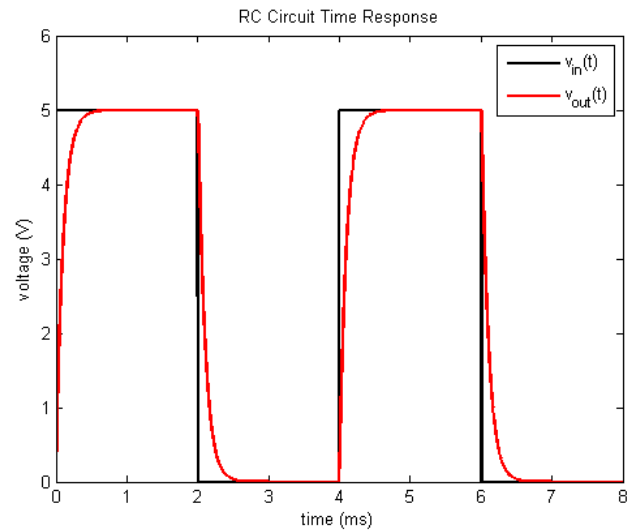

VIII. PRELAB#8

a) Figure 3.1.1: $\tau = RC$


b) Figure 3.1.2: $\tau = R_1(C_1 + C_2) + R_2C_2 = 3RC$

c) Figure 3.1.3: $\tau = R_1(C_1 + C_2 + C_3) + R_2(C_2 + C_3) + R_3C_3 = 6RC$

IX. PRELAB#9

$$v_{out} + RC \frac{dv_{out}}{dt} = V_0 \cos \omega t \quad (6)$$

X. PRELAB#10

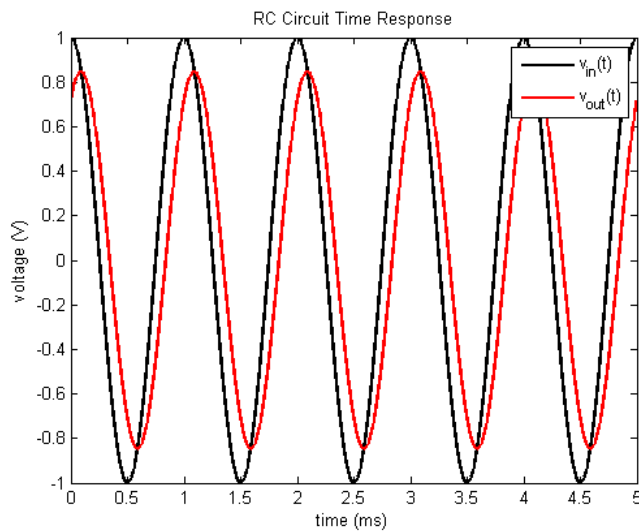


The output signal is a sinusoidal function.

The period $T = \frac{1}{f} = 1\text{ms}$

The magnitude $|v_{out}(t)| = \frac{v_0}{1+R^2C^2\omega^2} = 0.717$

XII. PRELAB#12

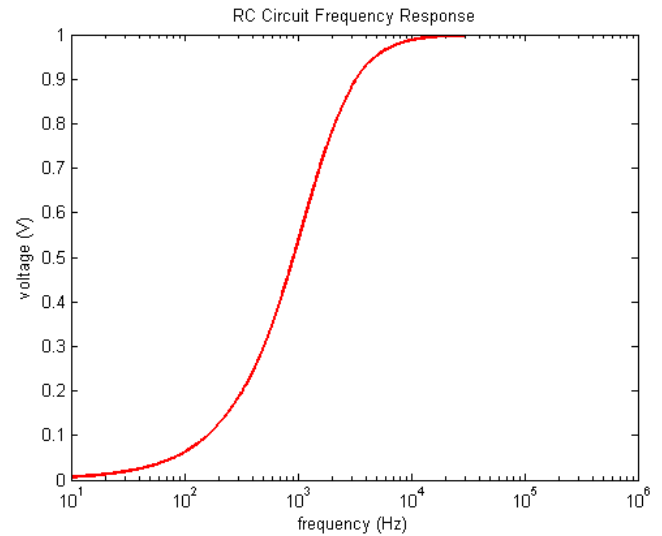

$$|v_{out}(1\text{Hz})| = 6.28 \times 10^{-4}$$


$$|v_{out}(1\text{MHz})| = 0.999$$

$$f \rightarrow 0, |v_{out}(f)| \rightarrow 0V$$

$$f \rightarrow \infty, |v_{out}(f)| \rightarrow V_0 = 1V$$

Explanation: the capacitor behaves like a low-pass filter while the resistor behaves like a high-pass filter. Because the sum of two voltages of R and C is v_{in} as a constant, their behaviors are just the opposite.

XI. PRELAB#11

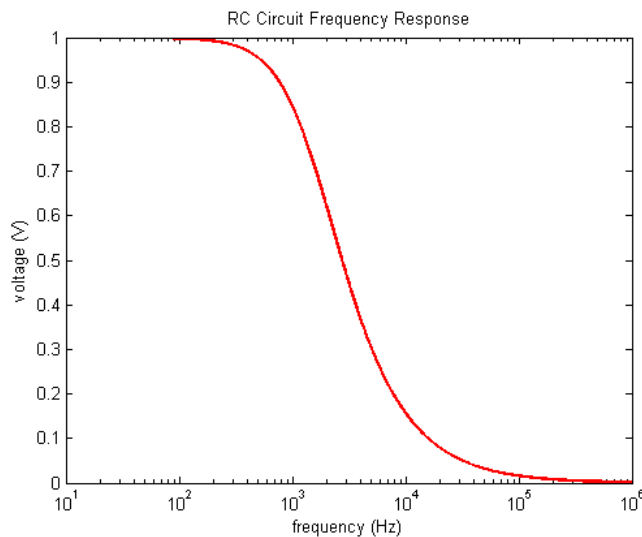

$$|v_{out}(10\text{Hz})| = 0.999$$

$$|v_{out}(1\text{MHz})| = 1.59 \times 10^{-3}$$

$$f \rightarrow 0, |v_{out}(f)| \rightarrow V_0 = 1V$$

$$f \rightarrow \infty, |v_{out}(f)| \rightarrow 0V$$